

Extracted from:

Essential 555 IC

Design, Configure, and Create Clever Circuits

This PDF file contains pages extracted from *Essential 555 IC*, published by the Pragmatic Bookshelf. For more information or to purchase a paperback or PDF copy, please visit <http://www.pragprog.com>.

Note: This extract contains some colored text (particularly in code listing). This is available only in online versions of the books. The printed versions are black and white. Pagination might vary between the online and printed versions; the content is otherwise identical.

Copyright © 2021 The Pragmatic Programmers, LLC.

All rights reserved.

No part of this publication may be reproduced, stored in a retrieval system, or transmitted, in any form, or by any means, electronic, mechanical, photocopying, recording, or otherwise, without the prior consent of the publisher.

The Pragmatic Bookshelf

Raleigh, North Carolina

The
Pragmatic
Programmers


Pragmatic
express

Essential 555 IC

Design, Configure,
and Create Clever Circuits

Cabe Force
Satalic Atwell

edited by Patrick DiJusto

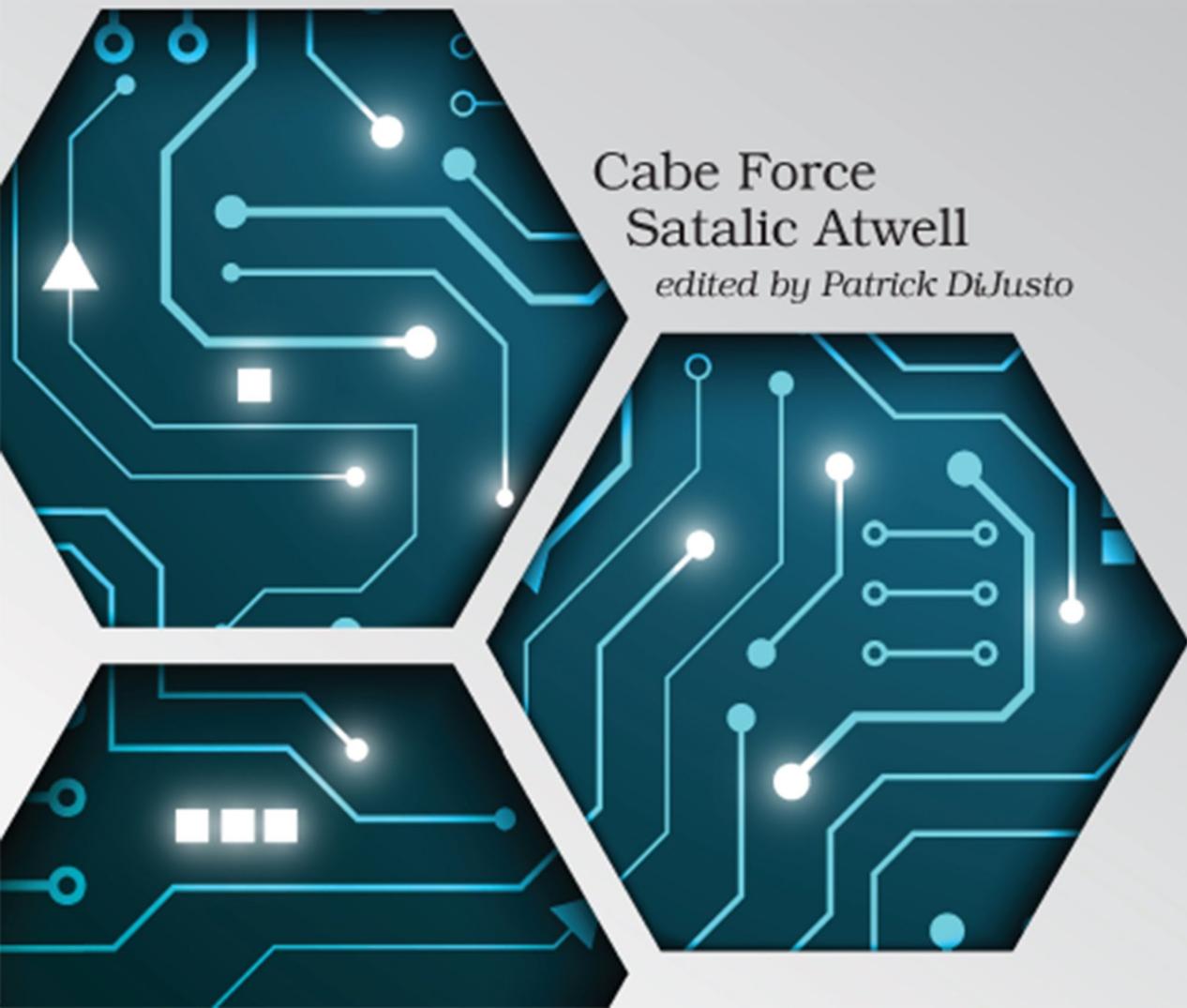

Essential 555 IC

Design, Configure, and Create Clever Circuits

Cabe Force Satalic Atwell

The Pragmatic Bookshelf

Raleigh, North Carolina



Many of the designations used by manufacturers and sellers to distinguish their products are claimed as trademarks. Where those designations appear in this book, and The Pragmatic Programmers, LLC was aware of a trademark claim, the designations have been printed in initial capital letters or in all capitals. The Pragmatic Starter Kit, The Pragmatic Programmer, Pragmatic Programming, Pragmatic Bookshelf, PragProg and the linking *g* device are trademarks of The Pragmatic Programmers, LLC.

Every precaution was taken in the preparation of this book. However, the publisher assumes no responsibility for errors or omissions, or for damages that may result from the use of information (including program listings) contained herein.

For our complete catalog of hands-on, practical, and Pragmatic content for software developers, please visit <https://pragprog.com>.

The team that produced this book includes:

CEO: Dave Rankin

COO: Janet Furlow

Managing Editor: Tammy Coron

Development Editor: Patrick Di Justo

Copy Editor: L. Sakhi MacMillan

Layout: Gilson Graphics

Founders: Andy Hunt and Dave Thomas

For sales, volume licensing, and support, please contact support@pragprog.com.

For international rights, please contact rights@pragprog.com.

Copyright © 2021 The Pragmatic Programmers, LLC.


All rights reserved. No part of this publication may be reproduced, stored in a retrieval system, or transmitted, in any form, or by any means, electronic, mechanical, photocopying, recording, or otherwise, without the prior consent of the publisher.

ISBN-13: 978-1-68050-783-6

Encoded using the finest acid-free high-entropy binary digits.

Book version: P1.0—April 2021

LED Brightness Dimmer

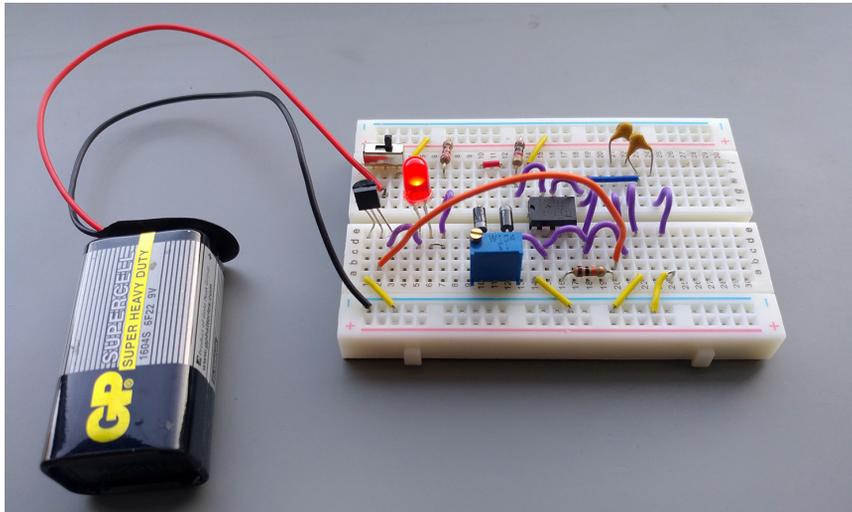

Learning how to dim an LED is as important as learning how to turn one on.

You might be wondering: “Are LEDs dimmable? Can I just use a potentiometer?” Sure you can, but with one caveat to that solution: when you lower the amount of electricity going to the LED using a resistor or potentiometer (variable resistor), all the excess energy gets converted to heat. Let’s say you have a 9 volt battery in the setup, and you want to dim a 2.1 volt LED. That means the potentiometer must dissipate nearly 7 volts of energy. Unless that potentiometer is huge, there’s a good chance it’s going to get really, really hot.

Deliberately designing a circuit that you know is going to heat up is dangerous for many reasons, so let’s defeat the heat. What you need is a way to reduce the amount of energy going to an LED without building up waste heat. The solution is something called *pulse width modulation*, also known as PWM.

In electronics, a *pulse* is a discrete burst of energy with a beginning, middle, and an end. When the pulse ramps up to peak voltage, the signal is said to be *high*. When the pulse reduces to zero, the signal is said to be *low*. The middle portion of the pulse, also known as the *width*, can last any amount of time: a fraction of a second, a few seconds, a minute, or an hour or more. The distance from one pulse to the next pulse is called a *duty cycle*. If the signal is at a peak voltage 100% of the time, it's called 100% duty cycle. Peak voltage only half the time is a 50% duty cycle, and so on.

To dim an LED, we *modulate*, or change the signal so that it's at peak voltage for only half the time and absolutely off for the other half of the time—a 50% duty cycle. This accomplishes our goal of reducing the amount of energy going to the LED, except that instead of reducing the voltage by half, we're reducing the time the LED is lit by half. Either way, the end result is that the LED appears only half as bright as it should.

Persistence of Vision

Obviously, if the LED's duty cycle is too long, you won't see a dimming effect, just a light blinking on and off. But because of the way the human eyes and nervous system work, an LED blinking at hundreds or thousands of times per second will be perceived as a dim LED. It's almost as if the brain averages an image of a fully lit LED and a fully dark LED into a mental image of a 50% lit LED.


By using pulse width modulation to dim an LED, no electrical power is wasted as heat, as it would be if we used a potentiometer.

Parts


555 Timer IC	Newark part number 58K8943	Jameco part number 27423
NPN Transistor, 2N3904	Newark part number 83C3116	Jameco part number 178597
LEDs of your choice. I suggest red.	Newark part number 52K5254	Jameco part number 206519
2x Diode, 1N4148	Newark part number 95W3791	Jameco part number 36038
220 Ω Resistor	Newark part number 38K0351	Jameco part number 690700
2x 1 k Ω Resistor	Newark part number 38K0327	Jameco part number 690865

This circuit can be used as an accessory in many of the other projects. You could use it to control the speed of a small motor like the kind you find inside old broken toys: just hook up the motor where the LED and resistor sit above the transistor.

Breadboard View

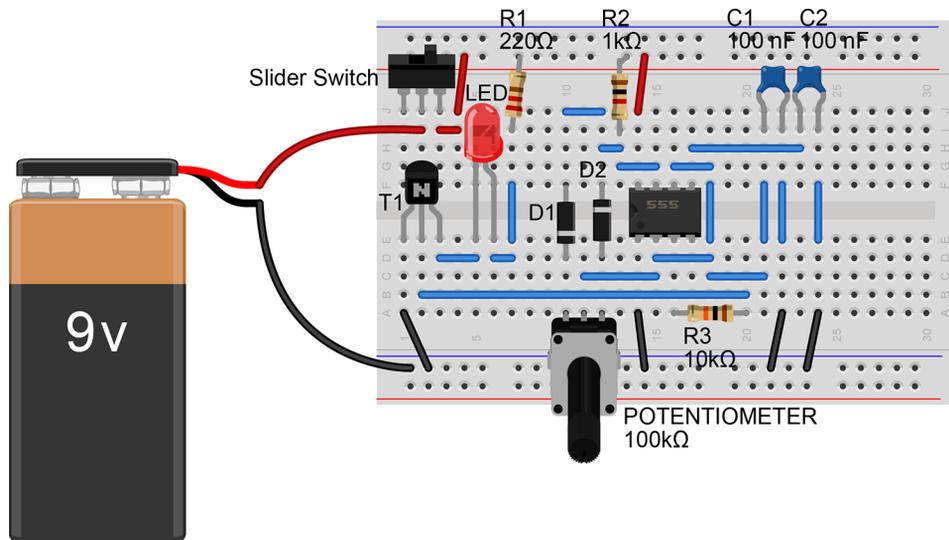

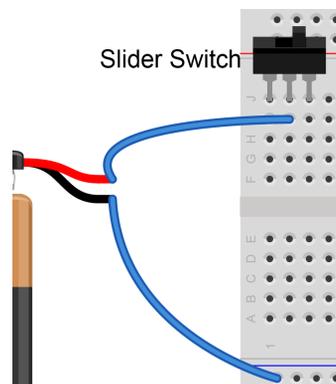This is the breadboard view. Again, pay close attention to the orientation of the diodes.



Place switch on the breadboard and connect positive lead on the battery to the middle pin on switch (common node).